Assignment -1 Tinkercad Circuit


Assignment Date	15 September 2022
Student Name	Mr. Sakthi Dasan B A
Student Roll Number	2019503555
Maximum Marks	2 Marks

Question:

Build a smart home in tinkercad

Solution:

Circuit Diagram:

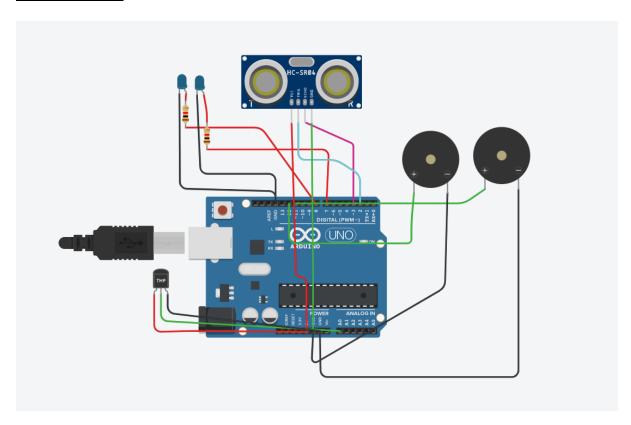


Source Code:

```
int t=2;
int e=3;
void setup()
 Serial.begin(9600);
 pinMode(t,OUTPUT);
 pinMode(e,INPUT);
 pinMode(12,OUTPUT);
}
void loop()
 //ultrasonic sensor
 digitalWrite(t,LOW);
 digitalWrite(t,HIGH);
 delayMicroseconds(10);
 digitalWrite(t,LOW);
 float dur=pulseIn(e,HIGH);
 float dis=(dur*0.0343)/2;
 Serial.print("Distance is: ");
 Serial.println(dis);
  //LED ON
 if(dis>=60)//(in terms of centimeter)
  digitalWrite(8,HIGH);
  digitalWrite(7,HIGH);
 }
 //Buzzer For ultrasonic Sensor
 if(dis>=60)
 for(int i=0; i<=5; i=i+1)
 tone(12,i);
 delay(1000);
 noTone(12);
 delay(1000);
 }
```


```
}
  //Temperate Sensor
 double a= analogRead(A0);
 double t=(((a/1024)*5)-0.5)*100;
 Serial.print("Temp Value: ");
 Serial.println(t);
 delay(1000);
 //LED ON
 if(t>=20)//(in terms of celsius)
  digitalWrite(8,HIGH);
  digitalWrite(7,HIGH);
 }
 //Buzzer for Temperature Sensor
 if(t>=20)
 for(int i=0; i<=5; i=i+1)
 tone(12,i);
 delay(1000);
 noTone(12);
 delay(1000);
 //LED OFF
 if(t<20)
  digitalWrite(8,LOW);
 digitalWrite(7,LOW);
}
}
```

Output:

• Serial Monitor:

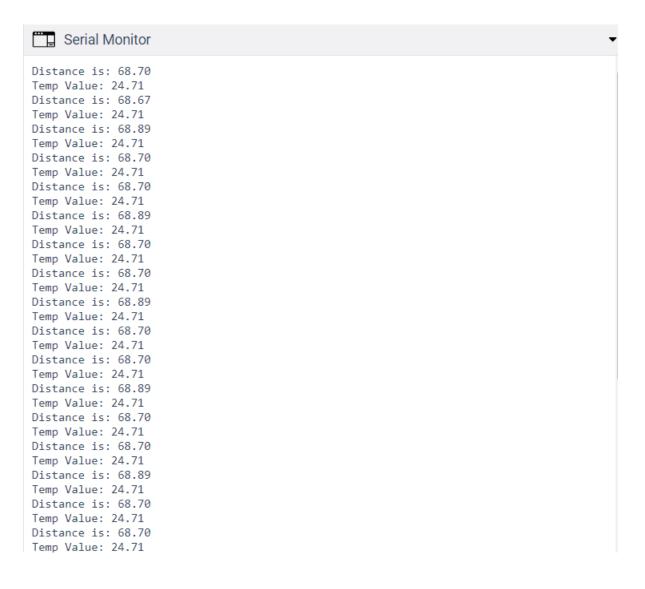

• Circuit Diagram:

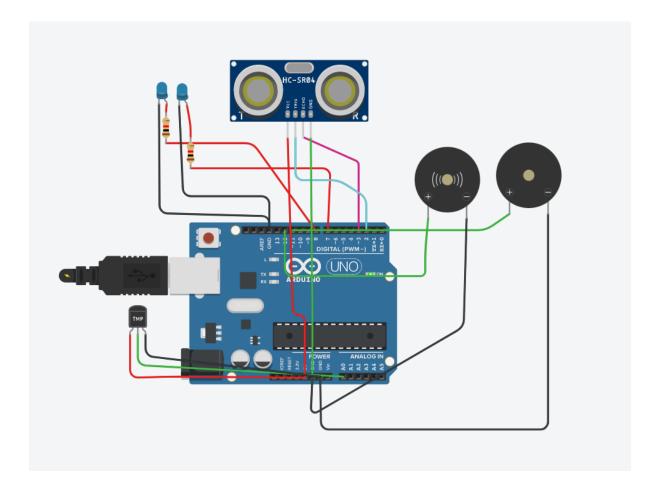

Tinkercad Link:

https://www.tinkercad.com/things/f7CMXFU13JU-ibm-assignment-1-smart-home/editel?sharecode=8L8ftnLaTN3dzkouSmt43CQjO7XNqdQ31LHnOy7lz7c